

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ETV/ECEII/COMP/CSE/IT/EEE/0664/2661/Nov'17**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Fill in the blanks.**

**1.5x10=15**

- a. The input impedance of a FET is \_\_\_\_\_ than that of BJT.
- b.  $I_{CEO} = \text{_____} I_{CBO}$ .
- c. The process of adding impurities is called \_\_\_\_\_.
- d. The turn on voltage in a silicon diode is \_\_\_\_\_.
- e. A zener diode is always operated in \_\_\_\_\_ region.
- f. Holes are \_\_\_\_\_ carriers in N-type semiconductors.
- g. When the gate terminal of MOSFET is positive it is said to operate in \_\_\_\_\_.
- h. The unit of  $h_{ie}$  is \_\_\_\_\_.
- i. In a transistor there are \_\_\_\_\_ PN junctions.
- j. The point of intersection of dc and ac load line is called \_\_\_\_\_.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x6=30**

- i. What is ripple factor? How it can be minimized?
- ii. Explain zener diode as a voltage regulator.
- iii. Explain intrinsic and extrinsic semiconductors.
- iv. Give construction and working of MOSFET.
- v. Explain the working of half wave rectifier.
- vi. Draw the circuit diagram of CE amplifier. Explain briefly.
- vii. What do you mean by h parameters of a transistor? Explain briefly.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Explain construction of NPN transistor. Explain how it can be used as amplifier.
- b. Discuss energy band structure for insulators, semiconductors and conductors.
- c. Write a short note on **(any two)**
  - i. Filter circuits
  - ii. AC and DC load line
  - iii. Avalanche breakdown
- d. What are various transistor biasing circuits? Compare their advantages and disadvantages.
- e. With the help of a diagram, explain the working of a bridge rectifier.

## BASIC ELECTRONICS

2<sup>ND</sup> Exam/ECE/ETV/ECEII/COMP/CSE/IT/EEE/0664/May'17

Duration: 3Hrs

M. Marks: 75

### SECTION A

Q.1 Fill in the blanks:

15x1=15

- N-type semiconductors are formed by adding \_\_\_\_\_ impurity to a pure semiconductor.
- In Intrinsic semiconductors number of electrons are \_\_\_\_\_ to number of protons.
- Conduction in P-type semiconductor is due to movement of \_\_\_\_\_
- The value of knee voltage for silicon diode is \_\_\_\_\_ volt.
- A Photodiode is optimised for its sensitivity to \_\_\_\_\_ .
- Zener diode is made to operate in \_\_\_\_\_ region.
- A transistor contains \_\_\_\_\_ PN junctions.
- The emitter of a transistor is doped \_\_\_\_\_.
- The value of collector current of a transistor is \_\_\_\_\_ to emitter current.
- In transistor, leakage current mainly depends on \_\_\_\_\_.
- The ideal value of stability factor is \_\_\_\_\_.
- The gain stability of an amplifier circuit can be improved by using \_\_\_\_\_ feedback.
- For a transistor to work as an amplifier, its operating point should lie in \_\_\_\_\_ region.
- FET is a \_\_\_\_\_ terminal semiconductor device.
- MOSFET stands for \_\_\_\_\_.

### SECTION-B

Q.2. Attempt any five Questions.

6x5=30

- How N-type semiconductor is formed?
- What are intrinsic and extrinsic semiconductors?
- Write a note on PN junction.
- What is Zener diode? Draw its symbol and explain its characteristics.
- What is transistor? Draw and explain PNP transistor.
- Differentiate between FET and BJT.
- What do you mean by thermal runaway?

### SECTION – C

Note: Attempt any three questions.

10x3=30

- Q3. What are needs of filter? Explain  $\pi$  (Pi) filter in detail.
- Q4. Derive an expression for amplification factor ( $\beta$ ) of common emitter configuration.
- Q5. What is CMOS? Explain its advantages and application.
- Q6. Explain the concept of bipolar transistor and draw symbol of NPN and PNP transistors.

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ECE-II/ETV/Comp/IT/CSc./EEE/0664/Nov'18**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Fill in the blanks.**

**15x1=15**

- a. The value of knee voltage of a Germanium diode is \_\_\_\_\_ volts.
- b. The electrons in the outermost orbit are called \_\_\_\_\_.
- c. Holes are \_\_\_\_\_ carriers in the p-type semiconductors.
- d. MOSFET is a \_\_\_\_\_ controlled device.
- e. A zener diode is always operated in \_\_\_\_\_ region.
- f. When pn junction is heavily doped, its breakdown voltage will be \_\_\_\_\_.
- g. FET is \_\_\_\_\_ polar device.
- h. The smaller the stability factor, the \_\_\_\_\_ will be the thermal stability of the circuit.
- i. If the arrow points outward, the transistor is an \_\_\_\_\_.
- j. The best biasing method is achieved by adopting \_\_\_\_\_ biasing circuit.
- k. BJT stands for \_\_\_\_\_.
- l. CMOS stands for \_\_\_\_\_.
- m. Current amplification factor of CB is \_\_\_\_\_.
- n. The meaning of hybrid is \_\_\_\_\_.
- o. Output signal frequency of full wave rectifier is \_\_\_\_\_ of input signal.

**SECTION-B**

**Q2. Attempt any six questions.**

**6x5=30**

- i. Explain the need for Stabilization of the Operating Point.
- ii. Discuss the advantages of FET over Conventional transistor.
- iii. Explain the effect of temperature on conductivity of intrinsic semiconductor.
- iv. Write a note on tunnel diode.
- v. Draw circuit of half wave Rectifier and explain its working. Draw the output waveform.
- vi. What do you mean by thermal runaway?
- vii. Draw and explain Filter Circuits.
- viii. What is Zener Diode? Explain its Applications.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Draw and Explain the Common emitter Configurations Characteristics.
- b. Explain construction and working principle of FET. Draw the neat diagram.
- c. Write note on PN Junction and its biasing. Difference between the n-type and p-type semiconductor.
- d. Explain in detail different types of biasing.
- e. Write short notes on the following. **(any two)**
  - i. LED
  - ii. Avalanche breakdown
  - iii. Schottky Diode

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ETV/ECE-II/COMP/CSE/IT/EEE/0664/May'18**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**15x1=15**

- a. N-type semiconductors are formed by adding ..... impurities to a pure semiconductor.
- b. Efficiency of half wave rectifier is .....
- c. Center-Tap transformer is used in ..... Wave rectifier.
- d. Filter circuits are used to reduce .....
- e. The value of knee voltage for silicon diode is ..... Volt.
- f. Zener diode is made to operate in ..... Region.
- g. In BJT, leakage current mainly depends on .....
- h. The point of intersection of dc and ac load line is called .....
- i. A.C. load line of a transistor is steeper than its D.C. load line. (T/F)
- j. The best biasing method is achieved by adopting ..... biasing circuit.
- k. JFET stands for .....
- l. MOSFET is a ..... Controlled device.
- m. The emitter and collector regions of BJT is ..... and ..... Doped.
- n. Free electrons exist in ..... band.
- o. When both the junctions of a transistor are forward biased, it is said to be in ..... region.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x6=30**

- i. Explain with suitable diagram Intrinsic and Extrinsic semiconductors.
- ii. What is Zener diode? Draw its symbol and explain its characteristics.
- iii. Explain the working of half wave rectifier.
- iv. Explain the working of NPN transistor.
- v. Explain the difference between FET and BJT.
- vi. What do you mean by h parameters of transistors?
- vii. In what way the temperature variations affect the operating point of a transistor?
- viii. Explain the phase reversal of output voltage with respect to input voltage in an amplifier.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Explain conductors, insulators and semiconductors on the basis of their energy band diagram.
- b. Draw circuit of a full wave bridge rectifier and explain its working. Draw the output waveform.
- c. Explain PN junction and draw the V-I characteristics of PN junction.
- d. Explain the input and output characteristics of CE configuration. Derive the relation between  $\alpha$  and  $\beta$ .
- e. Write a short note on **(any two)**
  - i. Light Emitting Diode
  - ii. Drift and Diffusion current
  - iii. Filter circuits.

S.B. Roll No.....

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ETV/ECE-II/COMP/CSE/IT/EEE/0664/May'19**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Fill in the blanks.**

**10x1.5=15**

- The larger the orbit, the \_\_\_\_\_ is the energy of electrons.
- Semiconductor material doped by \_\_\_\_\_ impurities is termed as n-type.
- The point of intersection of DC and AC load line is called \_\_\_\_\_.
- CMOS stands for \_\_\_\_\_.
- Transistor is a \_\_\_\_\_ terminal semiconductor device.
- Zener diode is made to operate in \_\_\_\_\_ region.
- MOSFET stands for \_\_\_\_\_.
- The process by which an impurity is added to semiconductor is called \_\_\_\_\_.
- The potential barrier voltage for Silicon is \_\_\_\_\_.
- The value of resistance of pn junction, when it is forward biased is \_\_\_\_\_.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x6=30**

- What do you mean by Zener Breakdown?
- Explain functioning of Half Wave Rectifier?
- Explain working of Transistors as an amplifier?
- What is the need of Stabilization of operating point?
- Explain working of LC Capacitor input filter?
- Explain p- type and n-type semiconductors?
- What is FET? Explain its working?

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- With the help of diagram, explain forward and reverse biased PN junction?
- Explain Bridge wave rectifier with circuit diagram?
- Differentiate between conductors, insulators and semiconductors on the basis of energy levels diagrams?
- Explain working of transistor with circuit diagram?

S.B. Roll No.....

**BASIC ELECTRONICS**  
**2<sup>nd</sup> Exam/ECE/CSE/IT/MECHATRONIC/0190/May'19**  
**(FOR 2018 BATCH)**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**15x1=15**

- a. Under normal operating voltages the reverse current in a silicon junction diode is in \_\_\_\_\_
- b. Ripple factor in full wave rectifier is \_\_\_\_\_
- c. CMOS means \_\_\_\_\_
- d. Write the relation between  $\alpha$  and  $\beta$ .
- e. Biasing in transistor is done to stabilize the \_\_\_\_\_
- f. At absolute zero temperature an intrinsic semiconductor behaves like \_\_\_\_\_
- g. In saturation region both junctions of transistors are \_\_\_\_\_ Biased.
- h. When a P-N junction is heavily doped its breakdown voltage will \_\_\_\_\_
- i. Operation of JFET involves \_\_\_\_\_ carriers.
- j. Boron has \_\_\_\_\_ valence electrons.
- k. An ideal diode has \_\_\_\_\_ forward resistance.
- l. The ideal value of stability factor is \_\_\_\_\_
- m. The communication path in an FET through which the carriers flow between drain and source is called \_\_\_\_\_
- n. A capacitor circuit does not allow passing \_\_\_\_\_ component.
- o. The material used for the construction of LED is \_\_\_\_\_ band gap.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x6=30**

- i. Compare the MOSFET and BJT.
- ii. Explain the behavior of P-N junction under different bias conditions.
- iii. Draw h- model of CE amplifier.
- iv. Describe the importance of load line with suitable diagrams.
- v. Explain the terms avalanche and zener breakdown.
- vi. Give advantages and applications of CMOS.
- vii. Derive the relation  $I_c = \alpha I_E + I_{CBO}$  and explain different terms used in them.
- viii. Write a note on drift and diffusion currents.
- ix. What is a filter circuit? Explain the working of LC filter.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Compare CB, CE and CC Configurations with at least five parameters.
- b. With the help of diagram and waveforms, Explain working of Center tap full wave rectifier.
- c. Explain the divider method of biasing for transistor (CE).
- d. Write a short note on any two of the following:
  - i. Thermal Runaway
  - ii. Varactor diode (Symbol, operation, application)
  - iii. BJT as an amplifier.
- e. Explain Construction, operation and characteristics of a MOSFET in depletion and enhancement modes.

S.B. Roll No.....

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ETV/ECE-II/COMP/CSE/IT/EEE/0664/Sep'2020**

**Duration: 1.15 Hrs.**

**M.Marks:25**

**SECTION-A**

**Q1. Attempt any three questions.**

**3x5=15**

- a. Classify different types of solids based on energy band diagrams.
- b. Discuss the advantages of FET over Conventional transistor.
- c. Explain single stage transistor amplifier in detail.
- d. Write a note on light emitting diode.
- e. Draw circuit of full wave Rectifier and explain its working. Draw the output waveform.
- f. What do you mean by thermal runaway?
- g. Draw and explain series inductor Filter Circuits.
- h. What is Zener Diode? Explain its Application as a voltage regulator.

**SECTION-B**

**Q2. Attempt any one question.**

**1x10=10**

- i. Draw and Explain the Common base Configuration Characteristics.
- ii. Explain construction and working principle of MOSFET. Draw the neat diagram.
- iii. Write note on PN Junction and its biasing. Difference between the n-type and p-type semiconductor.
- iv. Define biasing? Explain in detail any one type of biasing circuits.
- v. Write note on any two
  - a) Photo diodes
  - b) Zener breakdown
  - c) Faithful amplification

S. B. Roll. No.....

**BASIC ELECTRONICS**  
**2<sup>nd</sup> Exam/ECE/CSE/IT/MECHATRONICS/0190/Jun'2021**  
**(For 2018 Batch Onwards)**

**Duration: 1.15Hrs.**

**M.Marks:25**

**SECTION-A**

**Q1. Attempt any three questions.**

**3x5=15**

- i. Explain the types of Extrinsic Semiconductor.
- ii. Classify the solids on the basis of Energy band Diagram.
- iii. Draw the circuit diagram and explain the working of Half wave rectifier
- iv. Draw and explain the VI Characteristics of Zener Diode and its applications.
- v. Explain the functions of components used in the Filter circuits.
- vi. How transistor can work as an amplifier
- vii. What do you mean by (a) Saturation region (b) Cut off (c) Active Region?

**SECTION-B**

**Q2. Attempt any one question.**

**1x10=10**

- a. Draw and explain the input and output characteristics of Common Base. Derive the relation between alpha and beta.
- b. What is the various method of transistor biasing? Draw and explain the circuit diagram of base resistor biasing.
- c. Define operating point of a transistor. What do you mean by stabilization of operating point?
- d. Explain the working principle of FET Amplifier. How will you determine the drain characteristics of a FET?



S. B. Roll. No. ....

**BASIC ELECTRONICS**

**2<sup>nd</sup> Exam/ECE/ETV/ECE-II/COMP/CSE/IT/EEE/0664/Jun'2021**

**Duration: 1.15Hrs.**

**M.Marks:25**

**SECTION-A**

**Q1. Attempt any three questions.**

**3x5=15**

- i. Write a short note on Avalanche Breakdown.
- ii. What are advantages and disadvantages of full-wave rectifiers?
- iii. Define Drift and Diffusion currents.
- iv. What is stabilization and its need.
- v. Define DC and AC Load Lines.
- vi. What are advantages and disadvantages of FET's over BJT's?
- vii. Define H-Parameters and its significance.
- viii. Define P and N type semiconductor.

**SECTION-B**

**Q2. Attempt any one question.**

**1x10=10**

- a. Explain the circuit diagram of Single Stage Transistor Amplifier.
- b. Compare CC, CB and CE configurations.
- c. Draw and explain energy level diagram of conductors, insulators and semiconductors.
- d. Explain voltage divider biasing circuit.
- e. Explain working of NPN transistor.