

DIGITAL ELECTONICS

3rd Exam/0620/0262/ECE/ETV/ECE(II)/CSE/CSc/EEE/Nov'17

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

1.5x10=15

- a. A _____ signal varies continuously with time.
- b. The radix of octal number is _____.
- c. 1's complement of 111101 is _____.
- d. The number of states in Decade counter is _____.
- e. The Boolean expression for OR gate is _____
- f. In logic addition $A+A=2A$ (T/F)
- g. NOR and NAND gate can realize any logic function. (T/F)
- h. ASCII stands for _____.
- i. SIPO Stands for _____.
- j. SSI stands for _____.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. What is multiplexer? Draw the logic diagram of 4:1 multiplexer.
- ii. A seven bit Hamming code is received as 1011111. Check if it is correct. If not, find the correct code if even parity is used.
- iii. Draw the symbol and truth table for XOR gate and NAND gate?
- iv. Draw and explain full adder circuit.
- v. Differentiate between Analog and Digital signals.
- vi. Define Propagation delay, Bit rate and Power dissipation.
- vii. Write a note on shift register?
- viii. Convert the following
 - i) $(110101)_2 = ()_{10}$
 - ii) $(5CB8)_{16} = ()_2$

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Simplify four variable functions using K- map and implement the circuit
 $F = \sum m(0, 4, 12, 8, 9, 13, 7, 15)$
- b. Draw and explain working of JK flip flop.
- c. Explain the operation of Decade counter.
- d. Explain following.
 - i. Seven segment display
 - ii. Universal gate

S.B. Roll No.....

DIGITAL ELECTRONICS

3RD Exam/ECE/ECE-II/ETV/CSE/COMP/IT/EEE/0620/Nov'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- In a digital system, digital signal requires _____ channel bandwidth.
- Collection of 4 bits is called _____.
- Radix of octal number is _____.
- BCD numbers express each decimal digit as a _____.
- TTL stands for _____.
- An inverter is also known as _____.
- The XOR gate is sometimes referred to as _____.
- LSI & VLSI devices use _____ technology.
- A multiplexer changes _____ data into _____ data.
- To overcome race around condition _____ type of flip flop is used.
- A ripple counter is _____ sequential circuit.
- IC 74194 is _____ shift register.
- The fastest A/D Converter is _____.
- Draw symbol of XNOR.
- The 2's complement of 11001000 is _____.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- Convert each binary number to decimal
a) $(110011.11)_2$ b) $(101010.01)_2$ c) $(1000001.11)_2$
- Explain ASCII code and convert a binary 1001011 to gray code.
- What are the different error detection and correction codes?
- Discuss the characteristics of TTL Logic Family.
- Explain the laws related to Boolean algebra.
- Explain De Morgan's theorems.
- Difference between Combinational and Sequential Circuit.
- Design 4 bit ring counter.

SECTION-C

Note: Attempt any three questions.

3x10=30

Q3. Explain the universal property of NAND & NOR Gate.

Q4. Draw the Karnaugh Map for the following of four variables

- $F(A,B,C,D) = \sum m(0,1,2,3,4,5,10,11)$
- $F(A,B,C,D) = \sum m(2,3,6,7,10,11,14,15)$

Q5. Write a short note on the following. (any two)

- Half Adder
- DEMUX
- Dual slope A/D Converter.

Q6. Explain the working principle of JK Master/ Slave flip flop and its truth table.

Q7. Explain Serial to Parallel Shift Register.

DIGITAL ELECTRONICS

3RD Exam/ECE/ETV/ECEII/Comp/CSc/EEE/0620/May'17

Duration: 3Hrs

M.Marks:75

SECTION- A

Q1. Do as directed:

15x1=15

- The numbers of levels in a digital system are _____.
- 1011 is a valid BCD number. (T/F)
- Binary code of gray code 1011_{gray} is _____.
- The expression $A.B$ represents _____ gate.
- The clear signal is same as reset signal.(T/F)
- The fastest ADC is _____.
- The maximum count in a 4-bit ripple counter is _____.
- To convert a JK flip-flop into T flip-flop, the inputs $J=K=$ _____.
- The condition $S=R=1$ is called as _____ condition.
- The complement of Boolean algebra AB . $(BC+AC)$ is _____.
- The radix of octal number is _____.
- The parity is used for error detection and correction. (T/F)
- _____ logic family has maximum fan-out.
- ASCII is a _____ code.
- A universal shift register can shift register left or right. (T/F)

SECTION- B

Q2: Attempt any six questions.

6x5=30

- Draw symbol and truth table of NOT, NAND and OR gate.
- Convert the following: **A)** $62_{16} \times 36_{16}$ **B)** $341_8 = (?)_{10}$
- Define noise margin, propagation delay and fan-out.
- Compare all logic families and their characteristics.
- Explain the operation of JK flip-flop using NAND gate.
- Explain dual slope A/D converter.
- Why universal shift registers are called universal? Explain.
- Draw and implement half adder.
- What are the applications of digital signal?

SECTION-C

Attempt any three questions

(3x10=30)

Q3. Simplify the given K-map and draw logic circuit using gates. $F(A,B,C,D) = \sum(0,3,6,7,9,13,14,15)$

Q4. Explain the working of 3-bit asynchronous counter.

Q5. Draw and explain BCD to decimal decoder. Give its applications also.

Q6. Write Short note on any two:

- 4-bit adder
- D/A converter
- Buffer register
- Latch and flip-flop

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/Comp/IT/CSc/EEE/0620/May'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

10x1.5=15

- Radix of Hexadecimal number is _____.
- ASCII code is _____ bit code.
- IC 7402 is _____ gate.
- BCD stands for _____.
- The expression $A+B$ represents _____ gate.
- 1011 is a valid BCD number. (T/F)
- 2's complement of 1101 is _____.
- CMOS stands for _____.
- 8:1 Multiplexer has _____ number of select lines.
- SSI stands for _____.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- What are advantages of digital signal?
- Draw and explain Half Adder.
- Explain the working of 3 bit asynchronous counter.
- Explain Universal gates with diagrams.
- Define noise margin, propagation delay and fan-out.
- Describe Ring counter with timing diagram.
- Explain the function of JK flip flop?
- Explain dual slope A/D converter.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- Draw symbol and truth table of various logic gates.
- Simplify the given K-map and draw logic circuit using gates:
 $F(A,B,C,D) = \sum(0,3,6,7,9,13,14,15)$
- Draw and explain BCD to decimal decoder. Give its applications also.
- Describe the operation of Universal Shift Register.
- Draw and explain the Full Subtractor.

S.B. Roll No.....

DIGITAL ELECTRONICS
3rd Exam/ECE/CSE/IT/0195/Nov'19
(FOR 2018 BATCH)

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

15x1=15

- a. 1's complement of 1001 is _____.
- b. Radix of a binary number is _____.
- c. The expression $A.B$ represent _____ gate.
- d. ASCII is _____ bit code.
- e. _____ signal varies continuously with time.
- f. $A+A=$ _____
- g. A Combinational Circuit does not have _____
- h. Race around condition can be avoided by using Master Slave JK Flip Flop. (T/F)
- i. A demultiplexer is a circuit with many inputs but only one output. (T/F)
- j. NAND and NOR gate can realize any logic function (T/F).
- k. SSI stands for _____
- l. BCD stands for _____
- m. CMOS stands for _____
- n. SIPO stands for _____
- o. Draw symbol of XOR gate

SECTION-B

Q2. Attempt any six questions.

6x5=30

- a. Draw and explain the circuit for Full Adder.
- b. Differentiate between analog and digital signal.
- c. Define Multiplexer. Explain 4:1 mux with the help of a diagram.
- d. Define shift register. Explain its types.
- e. Explain the universal property of NAND Gate
- f. Define Propagation delay and power dissipation
- g. Convert: - 1. $(25)_{10} = (?)_2$ 2. $(B3F5)_{16} = (?)_{10}$
- h. Differentiate between combinational and sequential circuit
- i. Describe the working of seven segment display.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- i. Explain construction and working of SR flip flop.
- ii. Define counter and explain the working of decade counter
- iii. Define Logic Gate. Explain its various types along with symbols and truth tables.
- iv. Simplify the function using K-map and implement the Circuit.
 $F = \sum m(0, 4, 12, 8, 9, 13, 7, 15)$
- v. Write short notes on the following.

a) ASCII Code

b) Parity

S.B. Roll No.....

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/CSE/Comp/IT/EEE/0620/May'19

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- Two's complement of 110101 is _____.
- Hexadecimal system uses digits from _____.
- Hamming code is a one type of _____ code.
- BCD stands for _____.
- Boolean rule $(A+B)(A+C) =$ _____
- Half adder is also known as _____.
- Flip flop is not a _____ circuit.
- Race around condition do not occur in _____ FF.
- Data is said to be in serial form if the bits are available _____
- Analog to digital conversion is _____ complex than digital to analog conversion.
- LCD consumes _____ power than LED display.
- RAM stands for _____.
- A _____ signal varies continuously with time.
- For decade counter no. of Flip-Flop required will be _____.
- A NAND gate acts as a _____ OR gate.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- Explain the Laws related to Boolean algebra.
- What do you mean by BCD codes? Explain.
- Explain operation of seven segment display.
- Explain various characteristics of standard TTL family.
- Explain RAM and ROM.
- Differentiate between a multiplexer and a Demultiplexer.
- Write down the application of A/D and D/A converter.
- Explain briefly the functioning of a serial in parallel out shift register.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- Explain the working and construction of dual slope ADC.
- Discuss the OR, AND, NOT, NAND, NOR gates with their symbols and truth tables.
- What is latch? Explain working principle of J-K master/slave flip flop and draw its truth table.
- Write short note on the following. **(any two)** i) Hamming Code ii) Parity iii) Ring counter
- Minimize and realize following logic functions using K-map
 $f(A, B, C, D) = \sum m(0, 1, 2, 5, 8, 9, 10)$

S.B. Roll No.....

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/CSE/EEE/0620/SEP'2020

Duration: 1.15 Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- Convert the following: i) $85.63_{10} = X_2$ ii) $300.45_{10} = (?)_8$
- Draw symbol and truth table of NAND gate.
- Define noise margin, propagation delay and figure of merit.
- List the difference between analog and a digital signal.
- Draw and explain asynchronous Mod-5 counter.
- What are shift registers? Give its types.
- Draw and explain 2:1 Multiplexer
- Draw and implement half adder.
- What are the applications of shift registers?

SECTION-B

Q2. Attempt any one question.

1x10=10

- Simplify the following K-map and draw logic circuit using gates.
 $F(A,B,C,D) = \sum(1,5,7,8,9,10, 11,14, 15)$
- Explain the working and construction of a successive approximation type of ADC.
- Draw and give truth table of JK flip-flop. What is race around condition in JK flip-flop? How it can be avoided.
- Write Short note on the following. a) decoder b) combination circuit c) parity

S. B. Roll. No.....

DIGITAL ELECTRONICS

3rd Exam/ECE/ETV/ECE-II/Comp/CSE/EEE/IT/0620/Jun'2021

Duration: 1.15Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- i. What are the advantages of Digital signals?
- ii. Describe NAND gate as universal gate.
- iii. Describe Ring counter.
- iv. Differentiate Weighted and non-weighted codes.
- v. Draw symbol and truth table of NOT, AND and NOR gate.
- vi. List the difference between combinational and a sequential circuits.
- vii. What are shift registers? Give its types.

SECTION-B

Q2. Attempt any one question.

1x10=10

- a. Simplify the following K-map and draw logic circuit using gates. $F(A,B,C,D) = \sum m(0,4,12,8,9,13,7,15)$
- b. Explain the working and construction of a dual slope type of ADC.
- c. Draw and give truth table of JK flip-flop. What is race around condition in JK flip-flop? How it can be avoided.
- d. Explain the working of 3-bit asynchronous counter.

S.B. Roll. No.....

DIGITAL ELECTRONICS
3rd Exam/ECE/IT/CSE/0195/Jun'2022
(For 2018 Batch Onwards)

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

15x1=15

- a. The no. of bits in a nibble is _____.
- b. Octal system uses digits from _____.
- c. Decimal 8 in excess-3 code is _____.
- d. $A + (B.C) =$ _____.
- e. BCD stands for _____.
- f. _____ changes serial data into parallel data.
- g. A Half adder adds _____ bits.
- h. _____ And _____ are UNIVERSAL gates.
- i. A flip flop is memory element. (T/F)
- j. EPROM is available in all technologies. (T/F)
- k. ASCII stands for _____.
- l. 4:1 Multiplexer has _____ number of select lines.
- m. Race around condition can be avoided by using Master Slave JK flip flop. (T/F)
- n. PIPO stands for _____.
- o. LED stands for _____.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. Differentiate between Analog and Digital signals?
- ii. Draw and explain the circuit for half subtractor?
- iii. Define SSI, MSI, LSI, VLSI and ULSI?
- iv. What is a T flip flop? Show its symbol and draw truth table for negative edge triggered T flip flop?
- v. Draw logic circuit of 4:1 multiplexer and explain its working?
- vi. Differentiate between asynchronous and synchronous counters?
- vii. Explain the working of decade counter?
- viii. Draw the circuit of parallel in-parallel out shift register and explain its working?

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Explain working and construction of JK flip flop. How Race around condition can be avoided by using Master Slave JK flip flop?
- b. Define logic gate? Explain various logic gates along with symbols and truth tables?
- c. Minimize and implement in SOP form
 $F(A, B, C, D) = \sum m(1, 2, 3, 6, 8, 12, 14, 15)$
- d. Draw and explain the circuit for half adder and full adder?
- e. Explain the following i) Universal shift registers ii) seven segment display